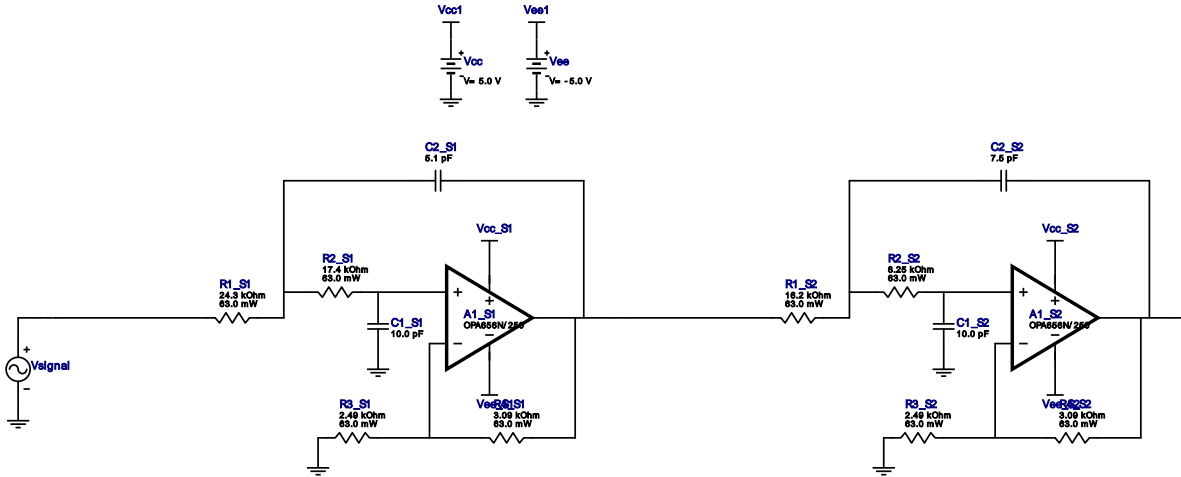


WEBENCH[®] Design Report

 Design : 3748350/3 OPA656N/250
 Lowpass, Sallen Key, Linear Phase 0.05deg


Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments	OPA656N/250	GbwTyp= 500.0 MHz VccMin= 7.0 V VccMax= 13.0 V	1	\$5.75	 SOT-23 14 mm ²
2.	A1_S2	Texas Instruments	OPA656N/250	GbwTyp= 500.0 MHz VccMin= 7.0 V VccMax= 13.0 V	1	\$5.75	 SOT-23 14 mm ²
3.	C1_S1	Kemet	C0402C100J3GACTU Series= C0G/NP0	Cap= 10.0 pF VDC= 25.0 V Tolerance= 5.0 %	1	\$0.01	 0402 3 mm ²
4.	C1_S2	Kemet	C0402C100J3GACTU Series= C0G/NP0	Cap= 10.0 pF VDC= 25.0 V Tolerance= 5.0 %	1	\$0.01	 0402 3 mm ²
5.	C2_S1	MuRata	GRM1555C1E5R1CA01D Series= C0G/NP0	Cap= 5.1 pF VDC= 25.0 V Tolerance= 5.0 %	1	\$0.01	 0402 3 mm ²
6.	C2_S2	MuRata	GRM1555C1H7R5CA01D Series= C0G/NP0	Cap= 7.5 pF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0402 3 mm ²
7.	R1_S1	Vishay-Dale	CRCW040224K3FKED Series= CRCW..e3	Res= 24.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
8.	R1_S2	Vishay-Dale	CRCW040216K2FKED Series= CRCW..e3	Res= 16.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
9.	R2_S1	Vishay-Dale	CRCW040217K4FKED Series= CRCW..e3	Res= 17.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
10.	R2_S2	Vishay-Dale	CRCW04028K25FKED Series= CRCW..e3	Res= 8.25 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
11.	R3_S1	Vishay-Dale	CRCW04022K49FKED Series= CRCW..e3	Res= 2.49 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
12.	R3_S2	Vishay-Dale	CRCW04022K49FKED Series= CRCW..e3	Res= 2.49 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
13.	R4_S1	Vishay-Dale	CRCW04023K09FKED Series= CRCW..e3	Res= 3.09 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
14.	R4_S2	Vishay-Dale	CRCW04023K09FKED Series= CRCW..e3	Res= 3.09 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

Design Inputs


#	Name	Value	Description
1.	FlatnessHigherTestFrequency	400.0	Magnitude Flatness Higher Test Frequency
2.	FlatnessLowerTestFrequency	0.0	Magnitude Flatness Lower Test Frequency
3.	FlatnessMagnitudeFlatnessSpecification	200.0 m	Flatness Specification
4.	GroupDelayFlatnessSpecification	100.0 m	Group Delay Flatness
5.	GroupDelayHigherTestFrequency	400.0	Group Delay Flatness Higher Test Frequency
6.	GroupDelayLowerTestFrequency	0.0	Group Delay Flatness Lower Test Frequency
7.	GroupDelaySpecification	510.0 m	Group Delay Specification
8.	FilterType	Lowpass	
9.	FilterResponse	Linear_Phase_005	
10.	FilterOrder	4.0	
11.	FilterTopology	Sallen_Key	
12.	NumberOfStages	2.0	
13.	PassbandFrequency	1000.0 k	
14.	StopbandAttenuation	-45.0	
15.	StopbandFrequency	5.0 M	
16.	Gain	5.0	
17.	DualSupply	+/-5.0 V	Power supply(s) to active chips
18.	ResistorTolerance	E96	Resistor series - 1% Passive resistor tolerance
19.	CapacitorTolerance	E24	Capacitor series - 5% Passive capacitance tolerance
20.	SeedCapacitance	10.0 p	Seed Capacitance to start design of filter

Design Assistance





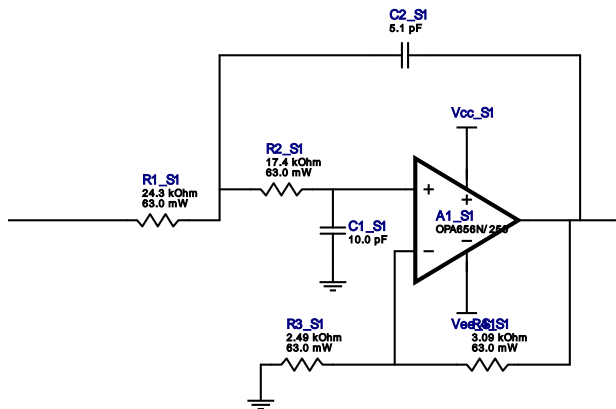


1. **OPA656N/250** Product Folder : <http://www.ti.com//product/OPA656> : contains the data sheet and other resources.

Filter Stage :1

Cutoff Frequency 1.075 MHz
 Min GBW Req'd 134.607 MHz
 Stage Gain 2.236 V/V
 Stage Q 560.0 m
 Stage Topology Sallen_Key




Electrical BOM





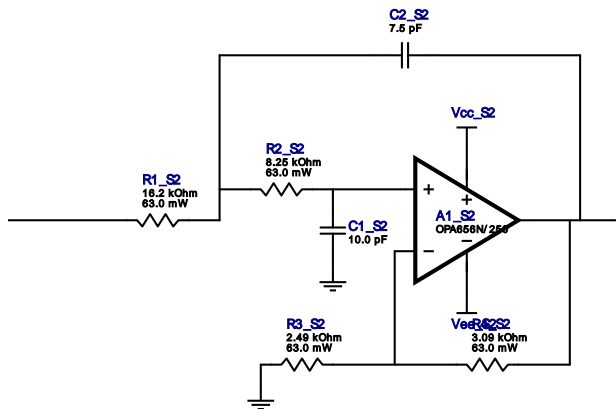

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments	OPA656N/250	GbwTyp= 500.0 MHz VccMin= 7.0 V VccMax= 13.0 V	1	\$5.75	 SOT-23 14 mm ²
2.	C1_S1	Kemet	C0402C100J3GACTU Series= C0G/NP0	Cap= 10.0 pF VDC= 25.0 V Tolerance= 5.0 %	1	\$0.01	 0402 3 mm ²
3.	C2_S1	MuRata	GRM1555C1E5R1CA01D Series= C0G/NP0	Cap= 5.1 pF VDC= 25.0 V Tolerance= 5.0 %	1	\$0.01	 0402 3 mm ²
4.	R1_S1	Vishay-Dale	CRCW040224K3FKED Series= CRCW..e3	Res= 24.3 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S1	Vishay-Dale	CRCW040217K4FKED Series= CRCW..e3	Res= 17.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
6.	R3_S1	Vishay-Dale	CRCW04022K49FKED Series= CRCW..e3	Res= 2.48 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
7.	R4_S1	Vishay-Dale	CRCW04023K09FKED Series= CRCW..e3	Res= 3.09 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

Filter Stage :2

Cutoff Frequency 1.586 MHz
 Min GBW Req'd 379.454 MHz
 Stage Gain 2.236 V/V
 Stage Q 1.07
 Stage Topology Sallen_Key



Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S2	Texas Instruments	OPA656N/250	GbwTyp= 500.0 MHz VccMin= 7.0 V VccMax= 13.0 V	1	\$5.75	 SOT-23 14 mm ²
2.	C1_S2	Kemet	C0402C100J3GACTU Series= C0G/NP0	Cap= 10.0 pF VDC= 25.0 V Tolerance= 5.0 %	1	\$0.01	 0402 3 mm ²
3.	C2_S2	MuRata	GRM1555C1H7R5CA01D Series= C0G/NP0	Cap= 7.5 pF VDC= 50.0 V Tolerance= 5.0 %	1	\$0.01	 0402 3 mm ²
4.	R1_S2	Vishay-Dale	CRCW040216K2FKED Series= CRCW..e3	Res= 16.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
5.	R2_S2	Vishay-Dale	CRCW04028K25FKED Series= CRCW..e3	Res= 8.25 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
6.	R3_S2	Vishay-Dale	CRCW04022K49FKED Series= CRCW..e3	Res= 2.49 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
7.	R4_S2	Vishay-Dale	CRCW04023K09FKED Series= CRCW..e3	Res= 3.09 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).